



BITS Pilani Digital Design

BITS Pilani
Pilani Campus



Prof. GSS Chalapathi, Prof. Saurabh Gandhi (EEE department)

Registers

- Flip-flops store only one bit
- We surely need larger units of storage, for example 32 bit integers or floating point numbers
- A register is an extension of a flip flop that can store multiple bits
- Registers are commonly used as temporary storage in a processors
 - Faster and more convenient than main memory
 - More registers can help speed up complex calculations

A basic register

  
- Basic registers are easy to build – just put a bunch of flip flops together!



Register with LOAD


- The input **D3-D0** is copied to the output **Q3-Q0** on *every* clock cycle.
- How can we store the current value for more than one cycle?
- Let's try to add a load input signal **LD** to the register.
 - If **LD = 0**, the register keeps its current contents.
 - If **LD = 1**, the register stores a new value, taken from inputs D3-D0.

LD	Q(t+1)
0	Q(t)
1	D ₃ -D ₀

 


LOAD with 'clock gating'

- We could implement the load ability by manipulating the **CLK** input, as shown below.
 - When **LD = 0**, the flip-flop C inputs are held at 1. There is no positive clock edge, so the flip-flops keep their current values.
 - When **LD = 1**, the **CLK** input passes through the OR gate, so all of the flip-flops will receive a positive clock edge and can load a new value from the **D3-D0** inputs.

 

The problems with clock gating


- This is called **clock gating**, since gates are added to the clock signal.
- There can be timing problems similar to those of latches. Here, LD must be kept at 1 for the right length of time (one clock cycle) and no longer.
- The actual clock signal is delayed a little bit by the OR gate.
 - In more complex circuits, different flip-flops might receive the clock signal at slightly different times.
 - This **clock skew** can lead to synchronization problems.

 


A better implementation of LOAD



 - Another idea is to modify the flip-flop D inputs and not the clock signal.
 - When $LD = 0$ the flip-flop inputs are $Q3-Q0$, so each flip-flop keeps its current value.
 - When $LD = 1$ the flip-flop inputs are $D3-D0$, so this new value is loaded into the register.




Parallel load without Muxes

 

Shift registers

 - A **shift register** "shifts" its output once every clock cycle. **SI** is an input that supplies a new bit to shift "into" the register.




$$\begin{aligned}
 Q0(t+1) &= SI \\
 Q1(t+1) &= Q0(t) \\
 Q2(t+1) &= Q1(t) \\
 Q3(t+1) &= Q2(t)
 \end{aligned}$$

- Here is one example transition.

Present State Q0-Q3	Input SI	Next State Q0-Q3
0110	1	1011

- The current Q3 (0 in this example) will be lost on the next cycle.

Shift direction

 

$$\begin{aligned}Q0(t+1) &= SI \\Q1(t+1) &= Q0(t) \\Q2(t+1) &= Q1(t) \\Q3(t+1) &= Q2(t)\end{aligned}$$

- The circuit and example make it look like the register shifts “right.”


Present Q0-Q3	SI	Next Q0-Q3
ABCD	X	XABC

- But it all depends on your interpretation of the bits. If you regard Q3 as the most significant bit, then the register appears to shift in the *opposite* direction!

Present Q3-Q0	SI	Next Q3-Q0
DCBA	X	CBAX

Shift registers with parallel load

 - We can add a parallel load operation, just as we did for regular registers.
 - When $LD = 0$ the flip-flop inputs will be $SIQ_0Q_1Q_2$, so the register will shift on the next positive clock edge.
 - When $LD = 1$, the flip-flop inputs are D_0-D_3 , and a new value is loaded into the register on the next positive clock edge.




The use of shift registers

Serial data transfer

- One application of shift registers is converting between serial data and parallel data.
- Computers typically work with multi-bit quantities.
 - ASCII text characters are 8 bits long.
 - Integers, single-precision floating-point numbers, and screen pixels are up to 32 bits long.
- But sometimes it's necessary to send or receive data **serially**, one bit at a time. For example, USB and Firewire devices such as keyboards, mice and printers all transfer data serially.


Receiving serial data

- You can convert serial data to parallel data using a shift register.
 - The serial device is connected to the register's **SI** input.
 - Shift register outputs **Q3-Q0** are connected to the parallel device.
- The serial device transmits one bit of data per clock cycle.
 - These bits go into the SI input of the shift register.
 - After four clock cycles, the shift register will hold a four-bit word.
- The computer then reads all four bits at once from the Q3-Q0 outputs.

 

Sending serial data


- To send data serially with a shift register, you can do the opposite.
 - The parallel device is connected to the register's **D3-D0** inputs.
 - The shift register output **Q3** is connected to the serial device.
- The computer first stores a four-bit word in the register, in one cycle.
- The serial device can then read the shift output.
 - One bit appears on Q3 on each clock cycle.
 - After four cycles, the entire four-bit word will have been sent.

 

Serial addition

- A second example using shift registers is adding two n -bit numbers with significantly less hardware than a standard adder.
- A four-bit ripple-carry adder contains four full adders, but note that the addition really happens serially, one step at a time.

 
1. Add $A_0 + B_0 + C_1$ to get S_0 and C_1 .
2. Add $A_1 + B_1 + C_1$ to get S_1 and C_2 .
3. Add $A_2 + B_2 + C_2$ to get S_2 and C_3 .
4. Add $A_3 + B_3 + C_3$ to get S_3 and C_0 .



Serial addition – implementation




- With shift registers, we can build an n -bit adder using only *one* full adder.
 - Inputs **A** and **B** are contained in shift registers.
 - Initially, the full adder computes $A_0 + B_0$.
 - On successive clock cycles, the values **A** and **B** are shifted to the right, so the adder computes $A_1 + B_1$, $A_2 + B_2$, etc.
 - The output **S** appears serially, one bit (S_0 , S_1 , S_2 , S_3) per cycle.

 

How to deal with the carry?

 - The carry out from one stage has to be added in the next stage.
- We need to add a D flip-flop as shown, so the carry out from one clock cycle is saved and used as the carry in for the next cycle.



Putting together the serial adder

- First, set **INIT = 1** for one clock cycle. This loads the initial values of A and B into the shift registers on top, and sets the D flip-flop to 0 (the initial carry in).
- When **INIT = 0**, the registers will begin shifting, and the full adder results will be written to register S one bit at a time.
- The addition is completed after four clock cycles. The sum is stored in S, and the carry out is in the D flip-flop.
- Notice how we get the **Shift Reg-4** in LogicWorks to shift in the proper direction.

Designing a serial adder from scratch



State Table for Serial Adder


Present State	Inputs		Next State	Output	Flip-Flop Inputs	
	x	y			J_Q	K_Q
0	0	0	0	0	0	X
0	0	1	0	1	0	X
0	1	0	0	1	0	X
0	1	1	1	0	1	X
1	0	0	0	1	X	1
1	0	1	1	0	X	0
1	1	0	1	0	X	0
1	1	1	1	1	X	0

$$J_Q = xy$$

$$K_Q = x'y' = (x + y)'$$

$$S = x \oplus y \oplus Q$$

 Serial adder from scratch implemented with shift registers



Universal shift register

